

## Structural Modeling CheatSheet (3-Bit Comparator)

© copyright 2018 v1.00

```
//- definition of XNOR gate
module my_xnor(A, B, F);
    input  A,B;
    output F;

    assign F = ~(A ^ B);
endmodule

//- definition of 3-input AND gate
module my_and(A, B, C, F);
    input  A, B, C;
    output F;

    assign F = A & B & C;
endmodule

//- definition of 3-bit comparator
module comp_3b(A,B,EQ);
    // external interface signals
    input [2:0] A,B;
    output EQ;

    // internal interface signals
    wire [2:0] m;

    // XNOR instantiations
    my_xnor XNOR2 (
        .A (A[2]),
        .B (B[2]),
        .F (m[2])    );

    // XNOR instantiation
    my_xnor XNOR1 (
        .A (A[1]),
        .B (B[1]),
        .F (m[1])    );

    // XNOR instantiation
    my_xnor XNOR0 (
        .A (A[0]),
        .B (B[0]),
        .F (m[0])    );

    // AND instantiation
    my_and  AND0 (
        .A (m[2]),
        .B (m[1]),
        .C (m[0]),
        .F (EQ)    );
endmodule
```

