

# CPE 133 Final Exam Cheat Sheet v1.03

		(AND)	(OR)	(XOR)
A	B	A•B	A+B	A XOR B
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	0









$$F(A,B,C) = \overline{\overline{(A)} + (B + C)} \quad (\text{reduced NOR/NOR})$$

## DeMorgan's

$$\overline{A \oplus B} = \overline{\overline{A}B} + AB \quad (\text{XNOR})$$

## Equivalent Signals

		(NAND)	(NOR)	(XNOR)
A	B	$\neg (A \bullet B)$	$\neg (A + B)$	$\neg (A \oplus B)$
0	0	1	1	1
0	1	1	0	0
1	0	1	0	0
1	1	0	0	1

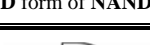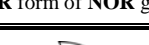AND functions	OR functions
	
AND form of AND gate	OR form of OR gate
	
AND form of OR gate	OR form of an AND gate
	
AND form of NAND gate	OR form of NOR gate
	
AND form of NOR gate	OR form of NAND gate

$t_{pd\_ff}$ : time for propagation delay in flip-flop

$$Frequency_{\max} = 1/T_{\min}$$

